

Logical Controls Lab 2 Preliminary task return


10.03.2025

Name: Pushpa Koirala Student ID: AG1715 Group: TAR24S1


Change the screenshots below to match your own implementation, so that the things hidden in the boxes are readable.

Please make sure that:

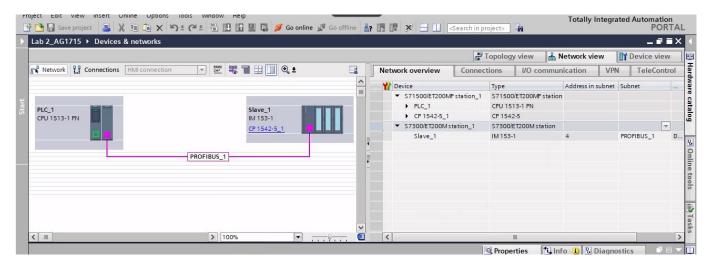- Your Student ID is visible in screenshots (in a project name)
- Screenshot quality is good
 - 1 Devices & networks view, to display CPU and ET200 Distributed IO:




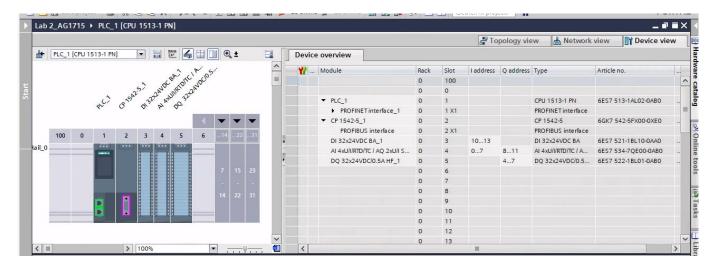2 Device configuration of **CPU** to show installed cards, including "Device overview" tab with addresses:






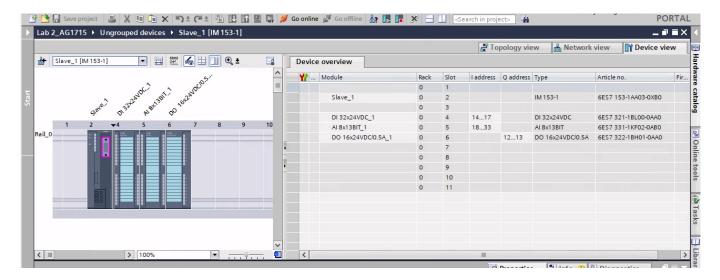3 Device configuration of **ET200 Slave_1** to show installed cards, including "Device overview" tab with addresses :






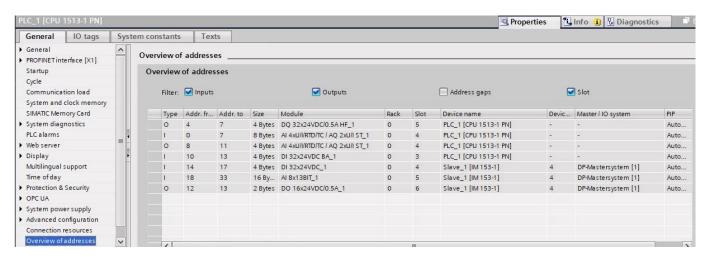
4 CPU Properties -> Overview of addresses:



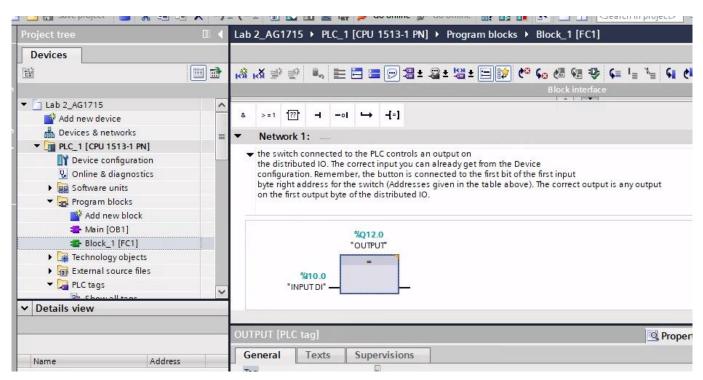5 Logic program (OB/FC) showing you are using the correct Input and Output addresses:



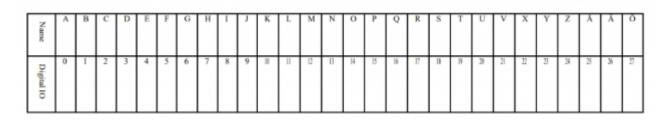6 Check that you have used the number corresponding to the first letter of your last name as the address of the digital input channel:





Your last name : Koirala

Digital input card address from table above : 10